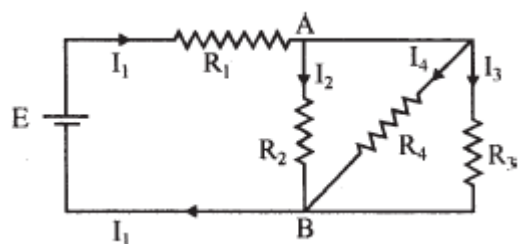


In the circuit shown, $R_1 = 4 \Omega$, $R_2 = R_3 = 15 \Omega$, $R_4 = 30 \Omega$ and $E = 10 \text{ V}$. Calculate the equivalent resistance of the circuit and the current in each resistor.



Answer

Given, $R_1 = 4 \Omega$, $R_2 = R_3 = 15 \Omega$, $R_4 = 30 \Omega$ and $E = 10 \text{ V}$

Here, R_2 , R_3 and R_4 are connected parallel to each other.

Therefore, equivalent resistance is given by,

$$\frac{1}{R} = \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}$$

$$= \frac{1}{15} + \frac{1}{15} + \frac{1}{30}$$

$\Rightarrow R = 6 \Omega$ is the effective resistance.

Now, R_1 is in series with R . So, equivalent resistance is given by,

$$R_{eq} = R + R_1$$

$$= 6 + 4$$

$$= 10 \Omega$$

Current I_1 is given by, $I_1 = \frac{E}{R_{eq}} = \frac{10}{10} = 1 \text{ A}$... (1)

This current is divided at A into three parts I_2 , I_3 , I_4 .

$$\therefore I_2 + I_3 + I_4 = 1$$
 ... (2)

Also,

Also,

$$I_2 R_2 = I_3 R_3 = I_4 R_4$$

$$\Rightarrow I_2 \times 15 = I_3 \times 15 = I_4 \times 30$$

$$\Rightarrow I_2 = I_3 = 2 I_4$$
 ... (3)

Physics
Now, putting the values of I_2 and I_3 in (2), we get



Current Electricity

$2I_4 + 2I_4 + I_4 = 1A$
Study, Assignments, Solved Previous Year Papers . Questions and Answers. Free Forever.

$$\Rightarrow I_4 = 0.2 \text{ A}$$

$$\therefore I_2 = I_3 = 2 \times 0.2 = 0.4$$

Thus, $I_1 = 1A$, $I_2 = I_3 = 0.4 \text{ A}$ and $I_4 = 0.2 \text{ A}$.